



# 전자 회로 2

## Lecture 11 (Stability)


---
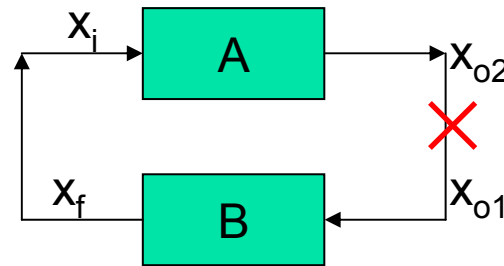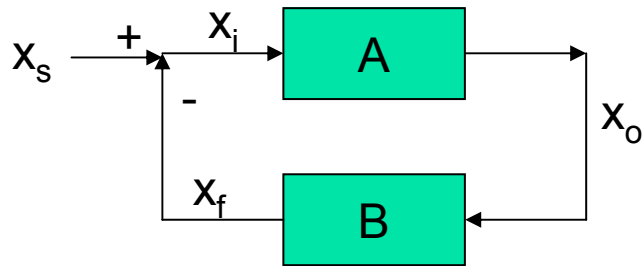
# Loop gain (AB)


- Loop gain:  $x_s=0$ 일 때의 gain
- Loop 중 아무곳이나 끊어도 gain은 언제나  $-AB$ 가 된다.



$$x_{o2}/x_{o1} = -AB$$

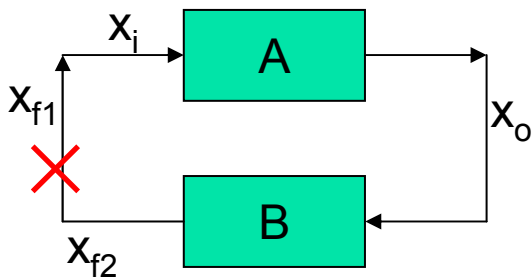


$$x_{f2}/x_{f1} = -AB$$

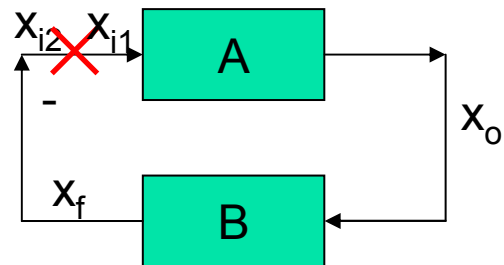


$$x_{i2}/x_{i1} = -AB$$


# Loop gain (Example)

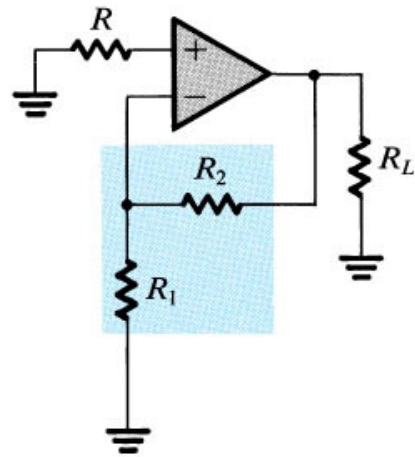

(a)

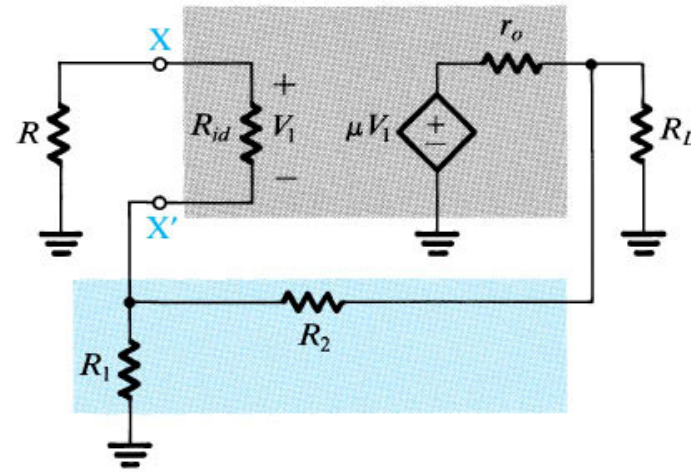

(b)

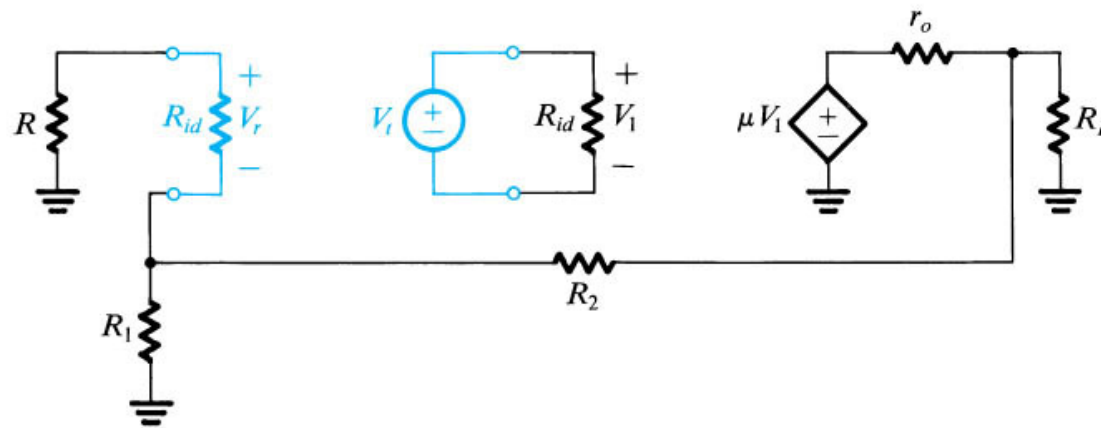

(c)

# Stability

- $x_s = 0$ 일 때 loop gain  $L(j\omega)$


$$A_f(s) = \frac{A(s)}{1 + A(s)B(s)}$$

$$\begin{aligned} L(s) &= A(s)B(s) \\ L(j\omega) &= A(j\omega)B(j\omega) \\ &= |A(j\omega)B(j\omega)|e^{j\phi(\omega)} \\ &= L(j\omega)e^{j\phi(\omega)} \end{aligned}$$

- $\phi(\omega) = 180^\circ$ 일 때  $L(j\omega) = -L_{180}$
- $L_{180} < 1 \rightarrow$  stable (noise reduction)
- $L_{180} \geq 1 \rightarrow$  unstable (noise enhancement)

- Nyquist plot


- 주파수에 따른 loop gain의 plot

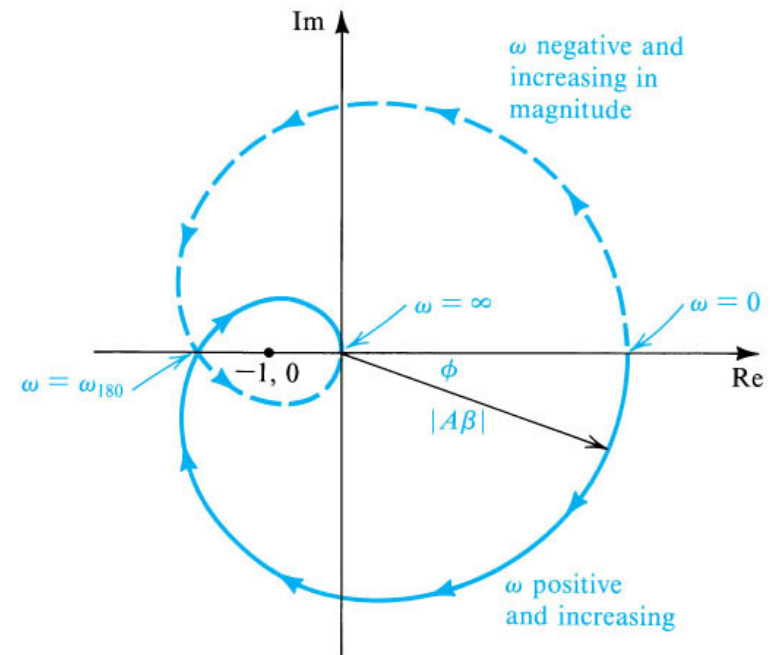
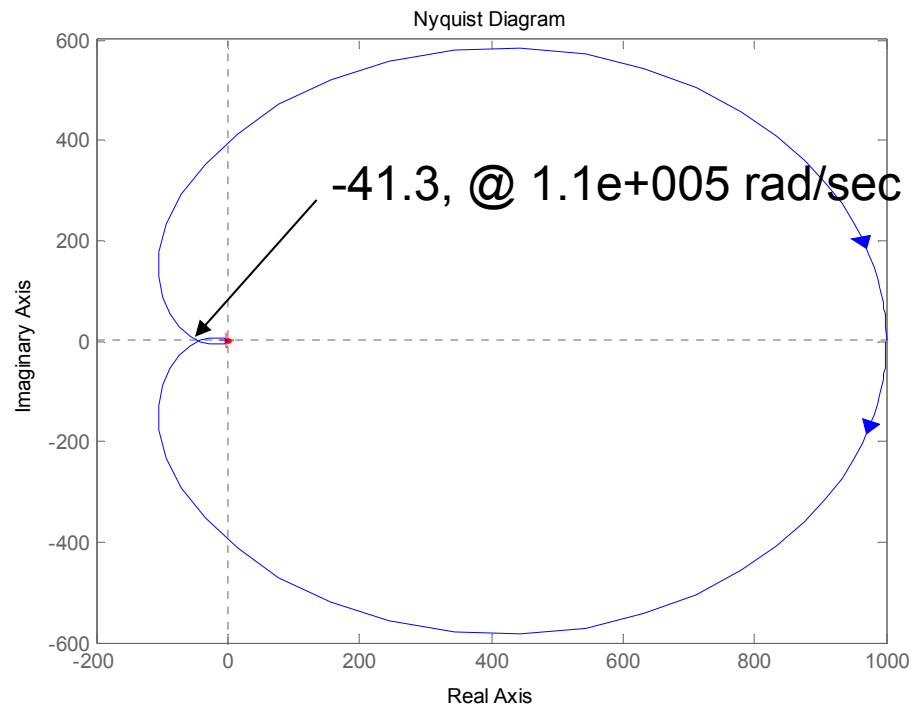
## Ex.) Problem 8.64

$$A(s) = \frac{1000}{(1 + s/10^4)(1 + s/10^5)^2}$$

```
> A = zpk([], [-10^4, -10^5, -10^5], 10^17);  
> nyquist(A)
```






Oscillation이 없으려면 AB의 nyquist plot이 Re축과 만나는 점이 -1보다 작아야 한다.

→  $B < 1/41.3$  → system이 안정

# Stability & pole location


- In  $s$ -domain (Laplace transform)

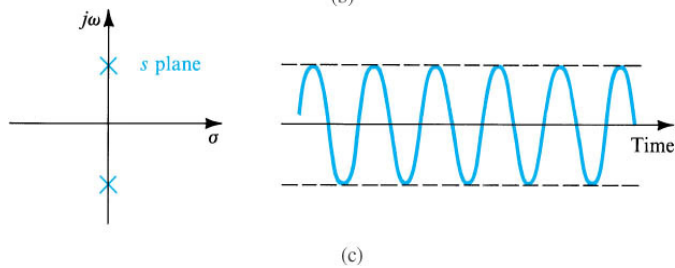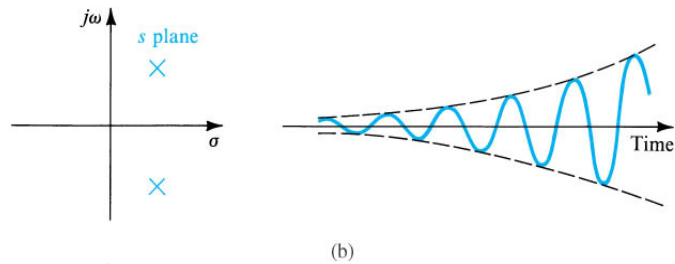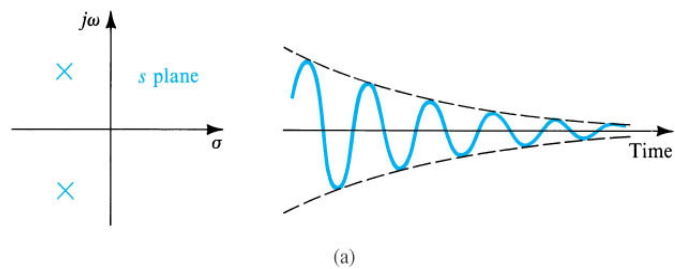

- Poles of a feedback amp.
- Characteristic equation
  - $1+A(s)B(s) = 0$
  - solution  $\rightarrow$  poles ( $s$ -domain)
- Pole이 left half plane에 있으면 시스템이 안정
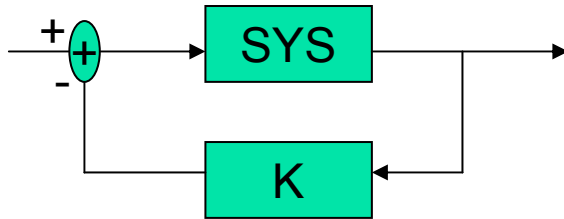
# Root Locus (rlocus)

RLOCUS(SYS) computes and plots the root locus of the single-input, single-output LTI model SYS. The root locus plot is used to analyze the negative feedback loop



and shows the trajectories of the closed-loop poles when the feedback gain  $K$  varies from 0 to  $\text{Inf}$ . RLOCUS automatically generates a set of positive gain values that produce a smooth plot.

RLOCUS(SYS,K) uses a user-specified vector  $K$  of gain values.

# Case 1) $A(s)$ has a single pole

$$A(s) = \frac{A_0}{1 + s/w_p}$$



$$A_f(s) = \frac{A_0/(1 + s/w_p)}{1 + A_0B/(1 + s/w_p)}$$

$$= \frac{A_0}{1 + A_0B + s/w_p}$$

$$= \frac{A_0}{1 + A_0B} \frac{1}{1 + s/w_p(1 + A_0B)}$$


$$w_{pf} = w_p(1 + A_0B)$$

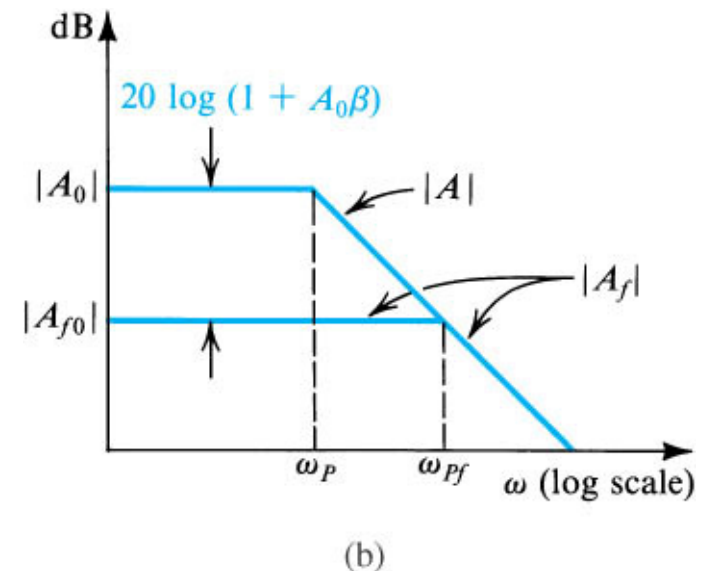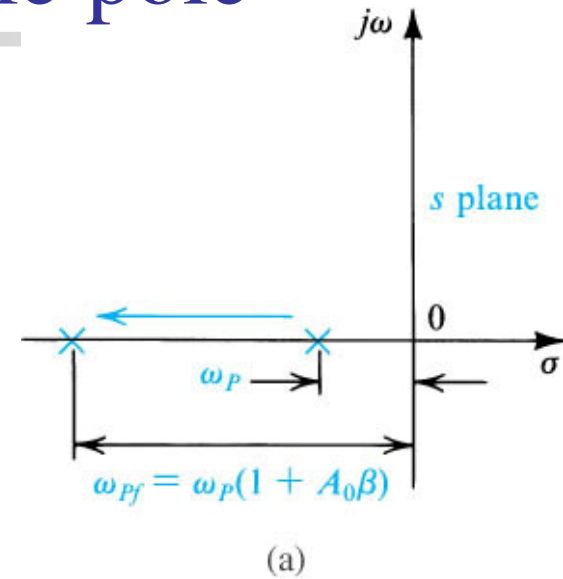If basic amp. is stable  
 → feedback is stable



> A = tf(1, [1, 1]);

> rlocus(A)

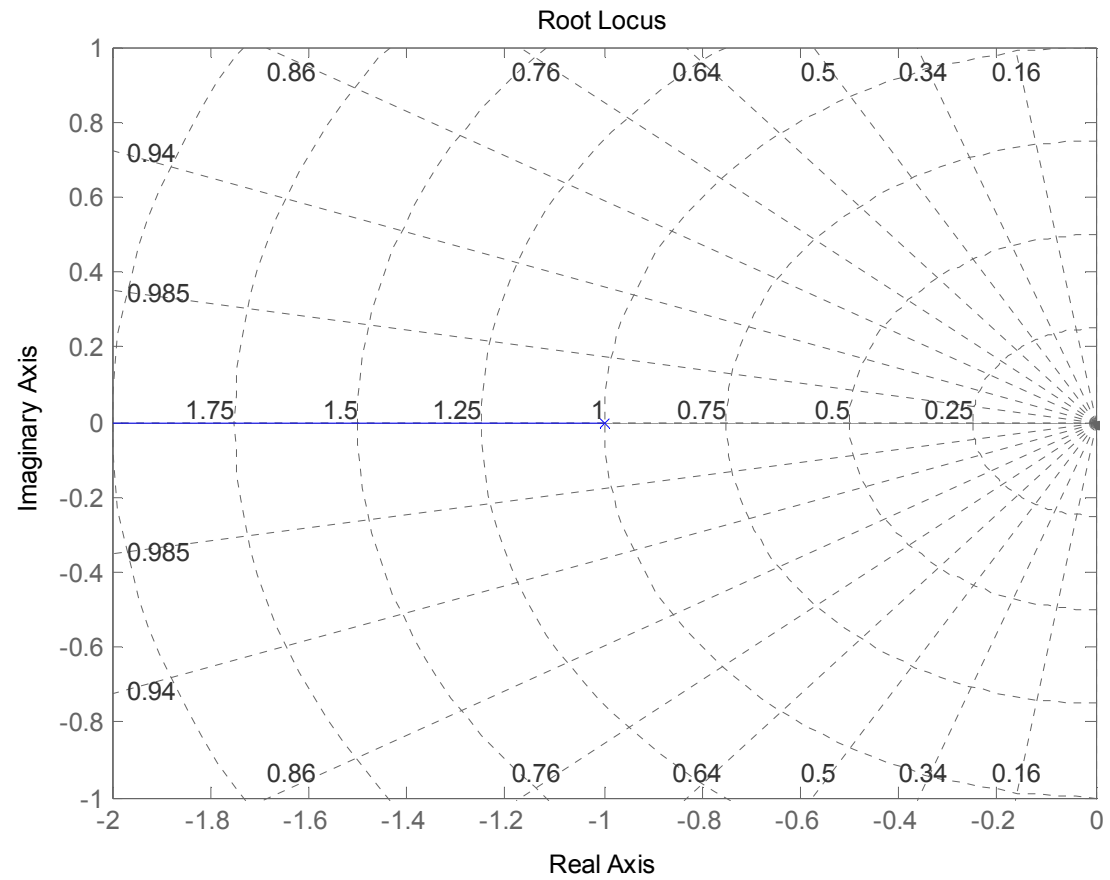


## Case 2) A(s) has two poles

$$A(s) = \frac{A_0}{(1 + s/w_{p1})(1 + s/w_{p2})}$$

$$s^2 + s(w_{p1} + w_{p2}) + (1 + A_0B)w_{p1}w_{p2} = 0$$
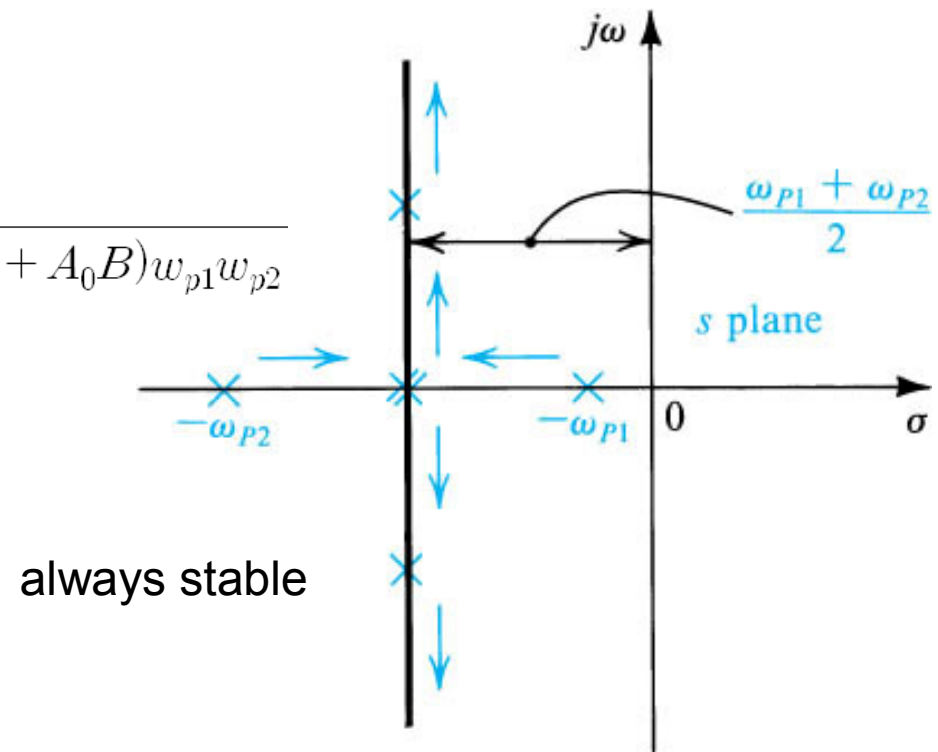
$$s = -\frac{w_{p1} + w_{p2}}{2} \pm \frac{1}{2} \sqrt{(w_{p1} + w_{p2})^2 - 4(1 + A_0B)w_{p1}w_{p2}}$$




root-locus diagram

AB를 키우면서 root를 그림




```
> A = zpk([], [-1, -2], 1);
```

```
> rlocus(A)
```

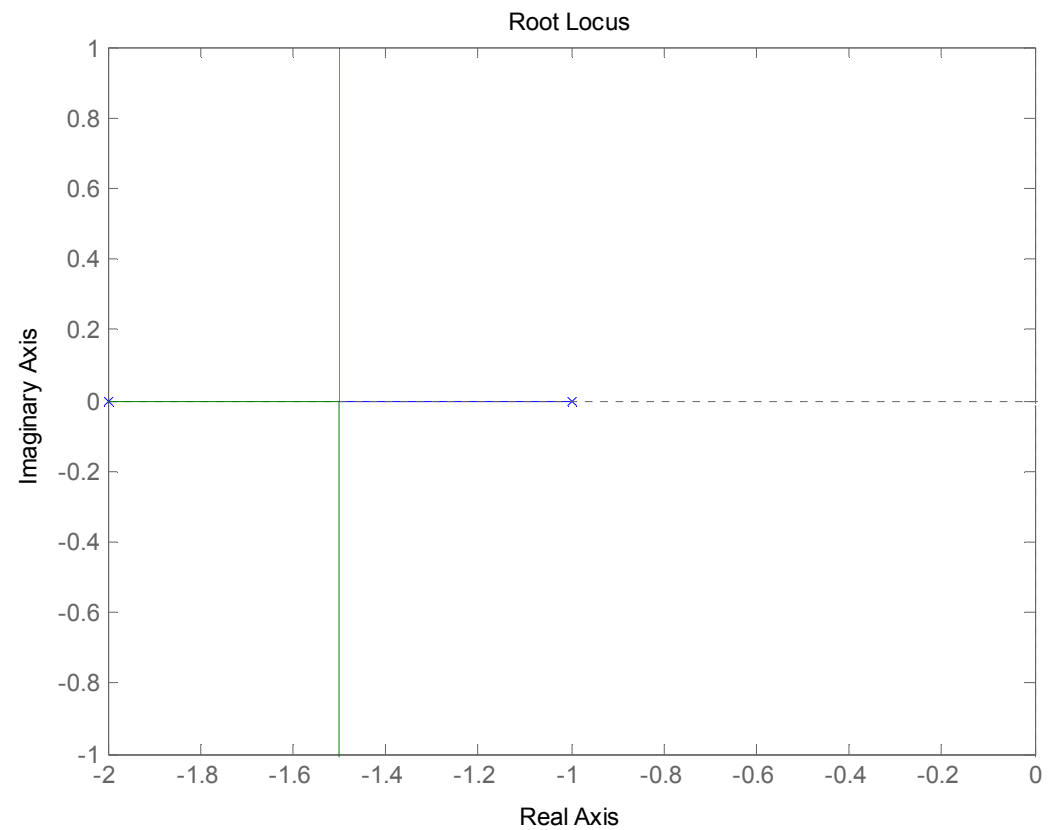


## Case 3) $A(s)$ has more than two poles

- Unstable 할 수 있음.

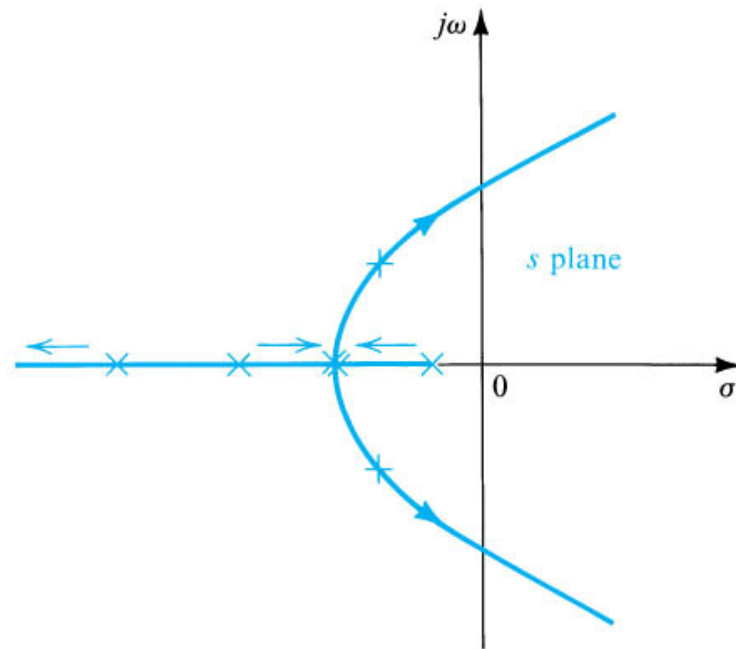
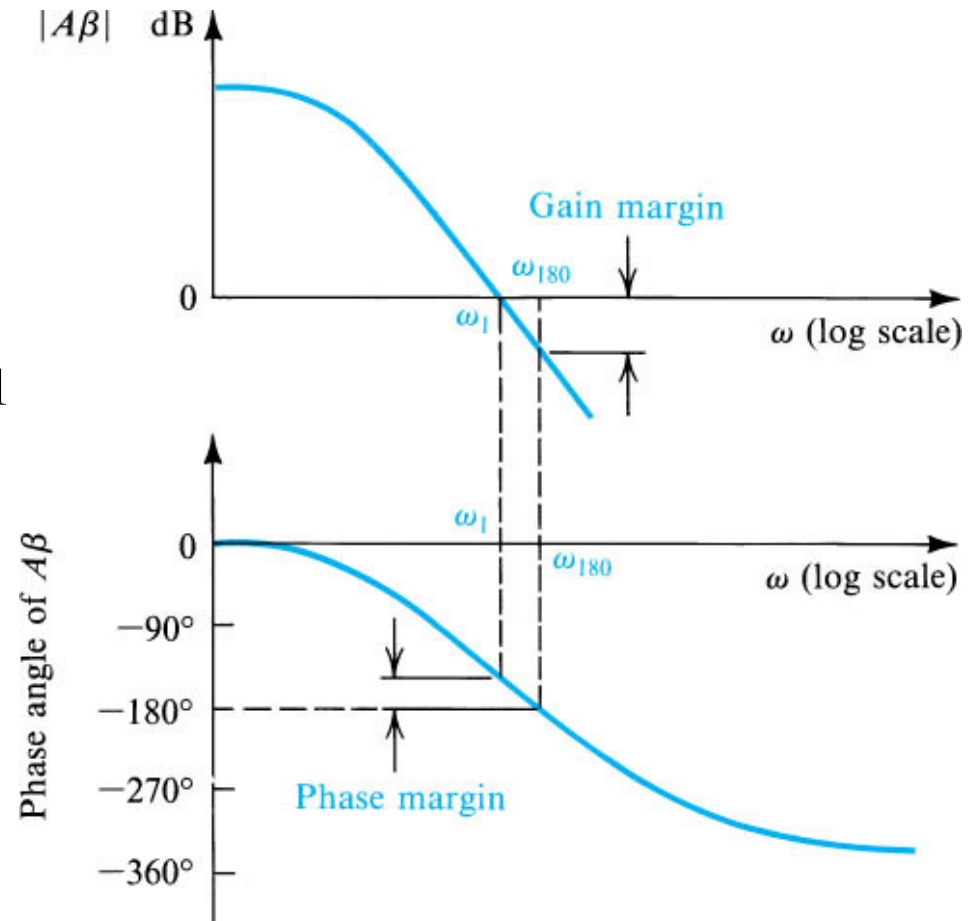
# Gain & Phase margin (Bode plot을 이용)


- Gain margin: phase가  $180^\circ$  일 때의 gain의 여유
  - dB로 표시
  - $GM > 0 \rightarrow$  stable
  - $GM < 0 \rightarrow$  unstable
- Phase margin: loop gain이 1 (0 dB)일 때  $180^\circ$ 에서의 phase의 여유
  - degree나 radian으로 표시
  - $PM > 0 \rightarrow$  stable
  - $PM < 0 \rightarrow$  unstable
- unstable일 경우 frequency compensation이 필요





```
> A = zpk([], [-10^4, -10^5, -10^5], 10^17);  
> bode(A)
```

Bode Diagram

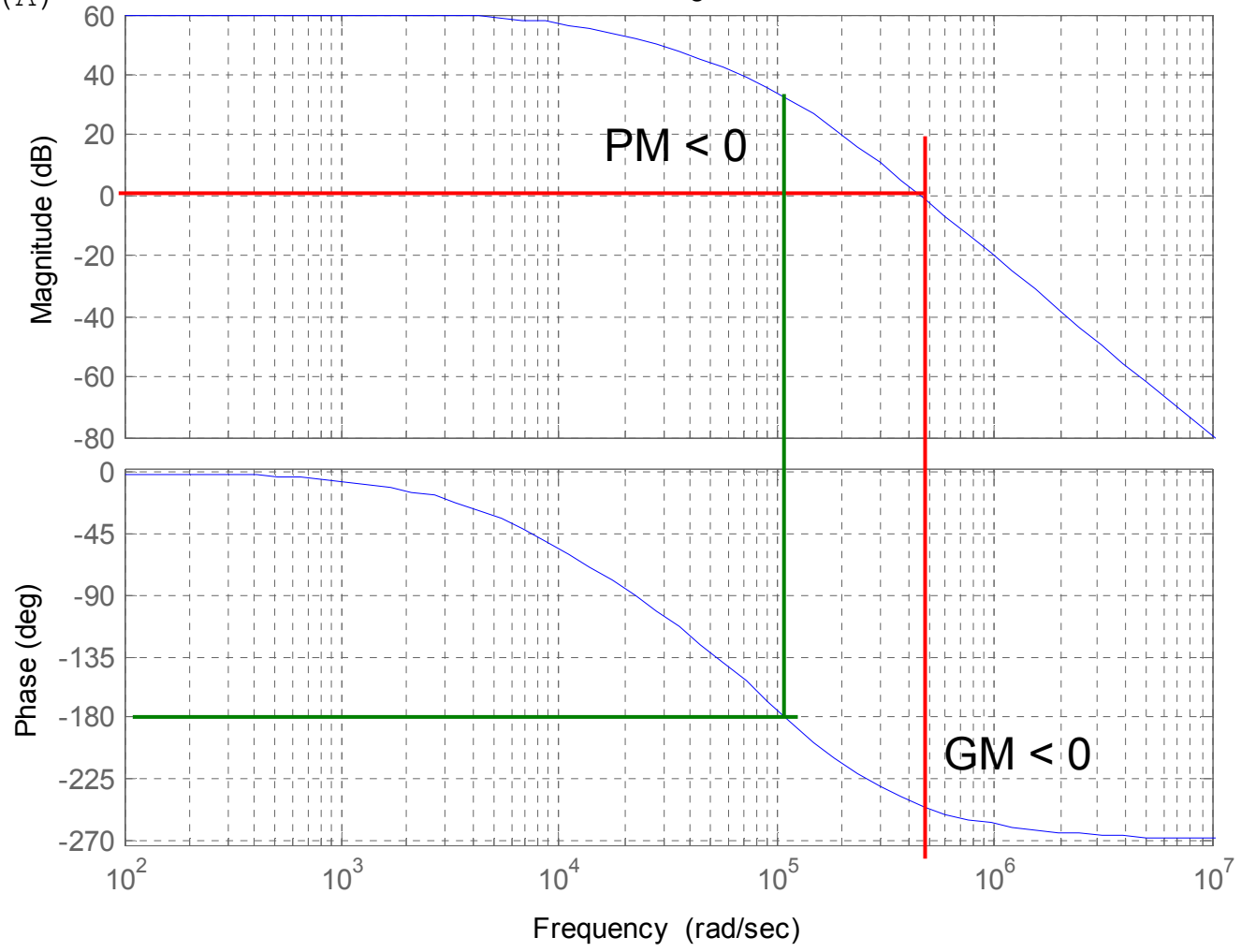



---

```
>> [Gm,Pm,Wcg,Wcp] = margin(A)
```

```
Warning: The closed-loop system is unstable.
```

```
> In lti.margin at 66
```

```
Gm =
```

```
0.0242 → GmdB = -32.32dB
```

```
→ B = 0.0242 = 1/41.3 → GmdB = 0
```

```
Pm =
```

```
-64.0575
```


```
Wcg =
```

```
1.0955e+005
```

```
Wcp =
```

```
4.5694e+005
```
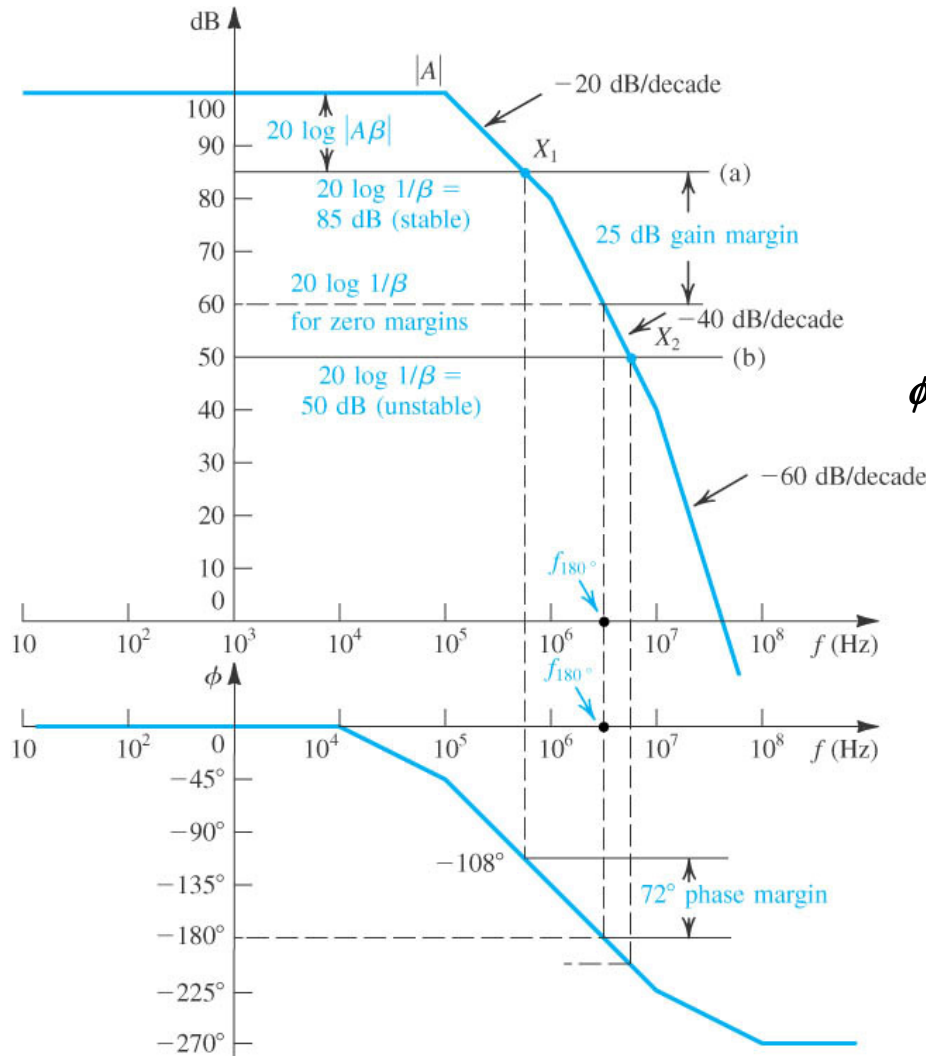
# Alternative approach ( $B(s) = B_0$ 일 때)



$$20 \log |A(j\omega)| - 20 \log \frac{1}{\beta} = 20 \log |A\beta|$$

$$A = \frac{10^5}{(1 + jf/10^5)(1 + jf/10^6)(1 + jf/10^7)}$$

$$\phi = -[\tan^{-1}(f/10^5) + \tan^{-1}(f/10^6) + \tan^{-1}(f/10^7)]$$




# Frequency compensation

---


- Negative feedback의 장점
  - Decreased distortion, noise reduction,
  - Increased bandwidth
  - Desirable  $R_{in}$ ,  $R_{out}$
- Negative feedback의 단점
  - Reduced gain
  - Possible instability
    - 해결책: Gain을 미리 줄인다.  
(phase=180도에서  $gain < 1$ 이 되도록)
    - $\beta$ 를 줄이는 법
    - 작은 Dominant pole을 놓는다. (pole splitting)

# Frequency compensation

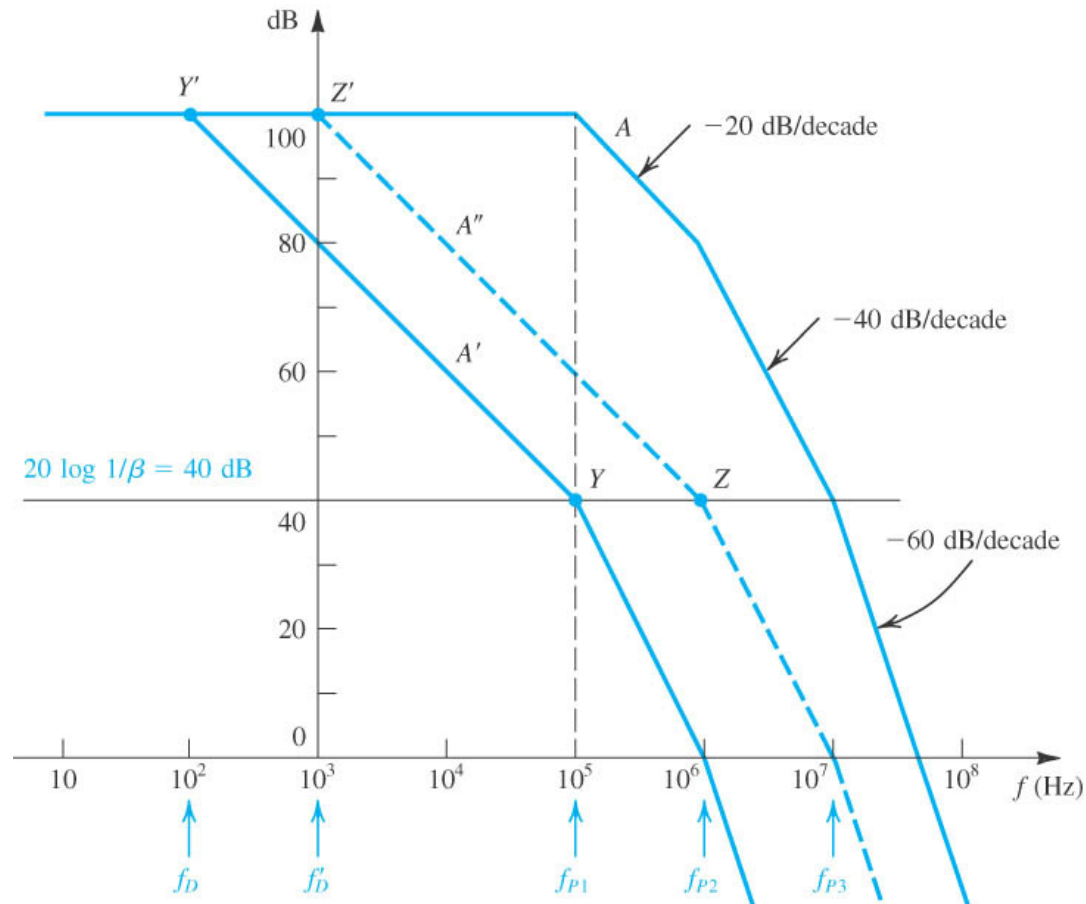


**Figure 8.38** Frequency compensation for  $\beta = 10^{-2}$ . The response labeled  $A'$  is obtained by introducing an additional pole at  $f_D$ . The  $A''$  response is obtained by moving the original low-frequency pole to  $f'_D$ .

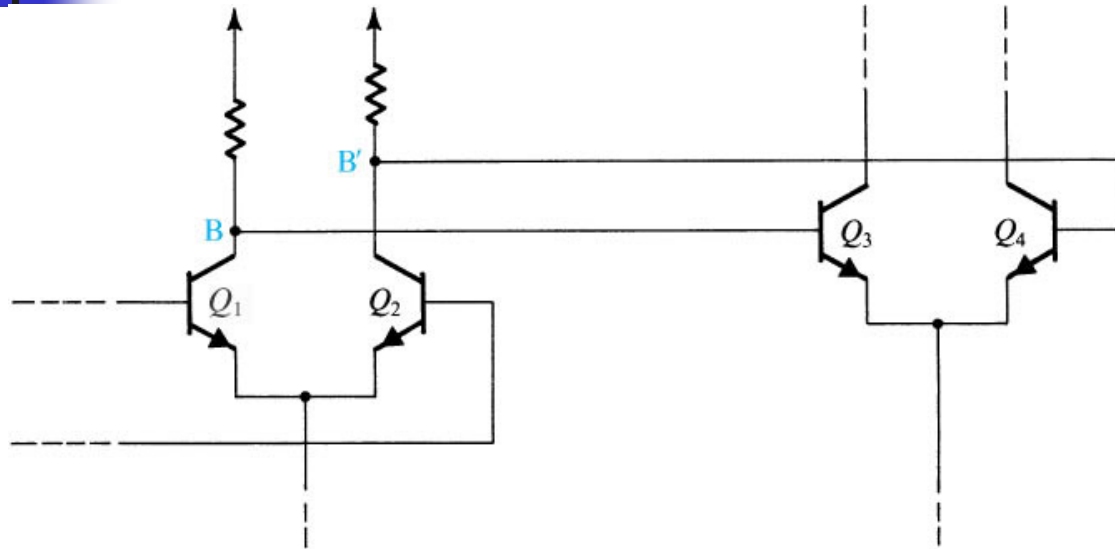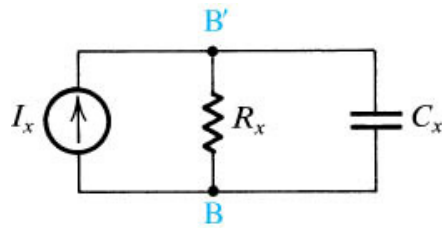
# Capacitance in-btw the differential inputs



(a)



(b)

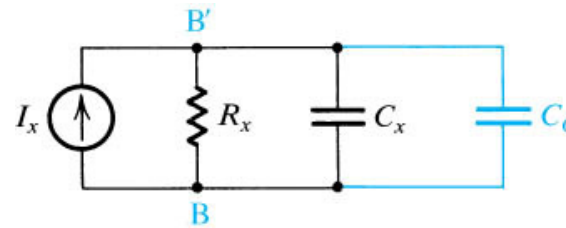


(c)

$$f_{p1} = \frac{1}{2\pi C_x R_x}$$

$$f_D' = \frac{1}{2\pi (C_x + C_C) R_x}$$


Large  $C_c$  required

# Miller compensation (feedback loop)

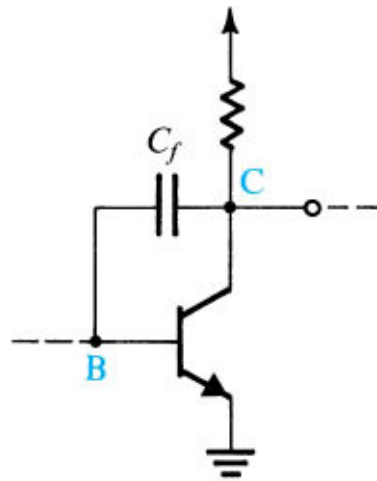

(a)

relatively small  $C_f$  required

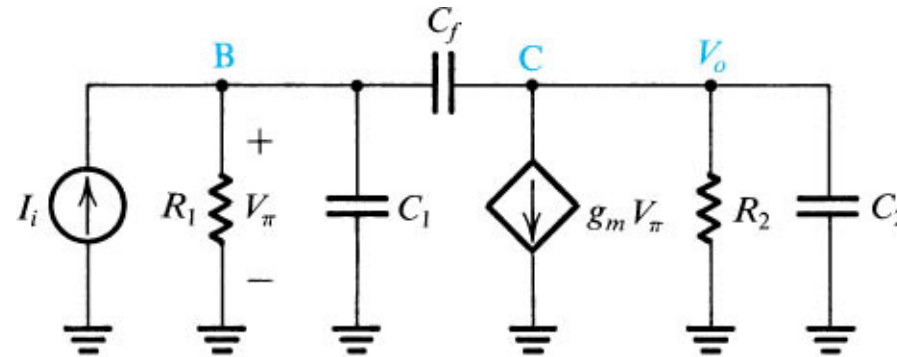

(b)

Without  $C_f$

$$f_{P1} = \frac{1}{2\pi C_1 R_1}$$

$$f_{P2} = \frac{1}{2\pi C_2 R_2}$$

With  $C_f$

$$\frac{V_o}{I_i} = \frac{(sC_f - g_m) R_1 R_2}{1 + s [C_1 R_1 + C_2 R_2 + C_f (g_m R_1 R_2 + R_1 + R_2)] + s^2 [C_1 C_1 + C_f (C_1 + C_2)] R_1 R_2}$$



With  $C_f$

$$D(s) = \left(1 + \frac{s}{\omega_{P1}'}\right) \left(1 + \frac{s}{\omega_{P2}'}\right) = 1 + s \left(1 + \frac{1}{\omega_{P1}'} + \frac{1}{\omega_{P2}'}\right) + \frac{s^2}{\omega_{P1}' \omega_{P2}'}$$

$$D(s) \approx 1 + \frac{s}{\omega_{P1}'} + \frac{s^2}{\omega_{P1}' \omega_{P2}'}$$

$$\omega_{P1}' = \frac{1}{C_1 R_1 + C_2 R_2 + C_f (g_m R_1 R_2 + R_1 + R_2)}$$

$$\omega_{P1}' \approx \frac{1}{g_m R_2 C_f R_1}$$

$$\omega_{P1}' \approx \frac{g_m C_f}{C_1 C_2 + C_f (C_1 + C_2)}$$

## EXAMPLE 8.6

$$f_{P1} = 0.1\text{MHz} = \frac{1}{2\pi C_1 R_1}$$

$$R_1 = \frac{10^5}{2\pi} \Omega$$

$$f_{P2} = 1\text{MHz} = \frac{1}{2\pi C_2 R_2}$$

$$R_2 = \frac{10^5}{\pi} \Omega$$

$$f_D' = \frac{1}{2\pi (C_1 + C_C) R_1}$$

$$f_D' = 10\text{Hz} = \frac{1}{2\pi (C_1 + C_C) R_1}$$

### EXAMPLE 8.6(cont'd)

$$f'_{P1} \square \frac{1}{2\pi g_m R_2 C_f R_1} \quad f'_{P2} \square \frac{g_m C_f}{2\pi [C_1 C_2 + C_f (C_1 + C_2)]} \quad (8.89)$$

$$f'_{P2} \square \frac{g_m}{2\pi (C_1 + C_2)} = 60.6 \text{ MHz}$$

$$f'_{P1} = \frac{f_{P3}}{A_0} = \frac{10^7 \text{ Hz}}{10^5} = 100 \text{ Hz}$$

$$f'_{P1} = 100 \text{ Hz} = \frac{1}{2\pi g_m R_2 C_f R_1}$$